 


Conventional System: simple switch

- **1 light: E1**
- **1 switch: S1**
 - Closed: current flow
 - Open: current interruption

S1	E1
Open	0
Closed	1




2 toggle switches

- 1 light: E1
- 2 toggle switches: S1, S2

S1	S2	E1
Left	Right	0
Left	Left	1
Right	Right	1
Right	Left	0

S1 & S2:

 
- on the same side: current flow
- on opposite sides: current interruption




Add a cross switch

S1	S2	S3	E1
Left		Left	1
Left		Right	0
Left	X	Left	0
Left	X	Right	1
Right		Left	0
Right		Right	1
Right	X	Left	1
Right	X	Right	0

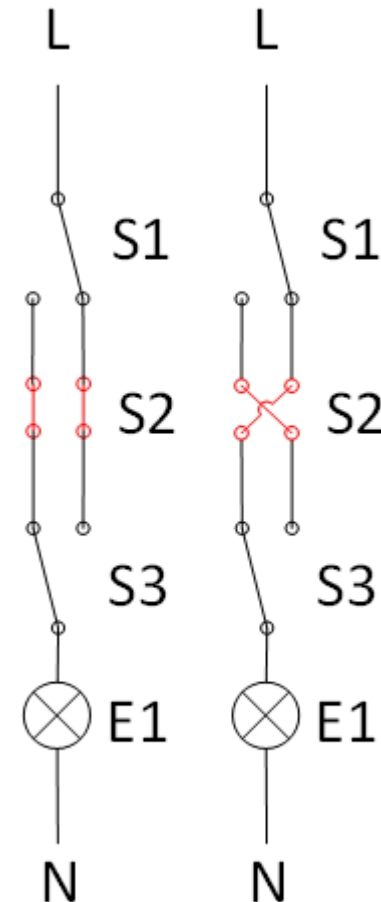
- **S1, S3 on the same side**
S2 'parallel': current flow
- **S1, S3 on opposite sides**
S2 'crossed': current flow



Add more cross switches

 


S2..Sn-1

 


Current flow if:

- **S1, Sn on the same side**
S2..Sn-1: #'crossed' connections = odd
- **S1, Sn on opposite sides**
S2..Sn-1: #'crossed' connections = even

Conventional System

 

S2..Sn-1

 


Functionality = hardwired

- S1 & Sn: 3 wires
- S2..Sn-1: 4 wires


Disadvantages:

- Cabling = complex = time consuming
- Unfavorable functionality/cable ratio
- Not flexible: adding switches = cumbersome
- No separation between power & operation

Hardwiring vs. ICT

 

S2..Sn-1

 


Alternative = ICT

Alternative = bus system


- Replace all switches by μ Cs
- Link the μ Cs via cable

Bus System = divided functionality

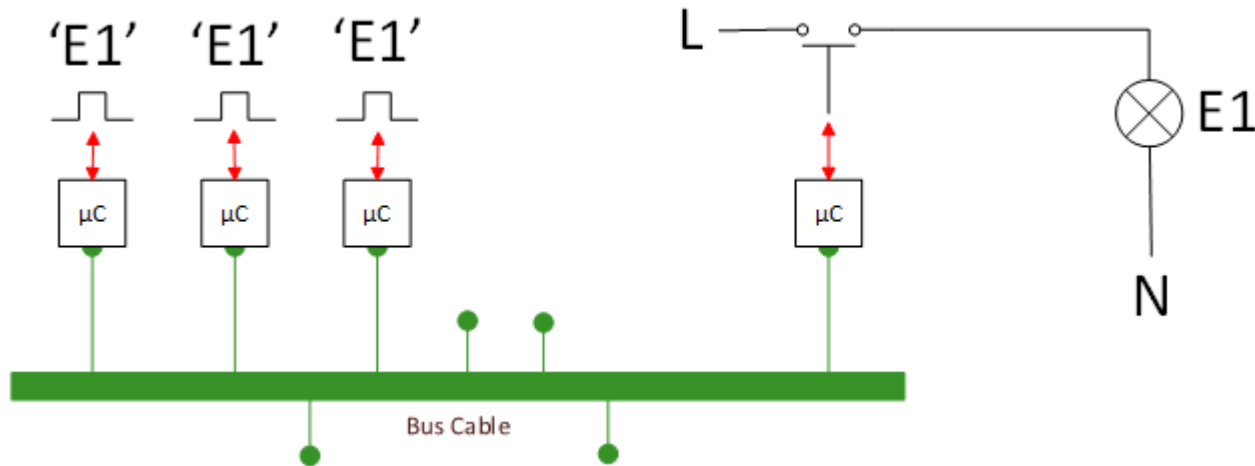

- **Sensors:** µC interfaced with e.g. a push button
- **Actuators:** µC interfaced with e.g. a relay
- Interfaced with = electronically connected to µC I/O ports
- Push buttons convert rocker manipulations into electronic pulses
- Relays switch electrical consumers indirectly via electronic pulses


Bus System = exchanging messages

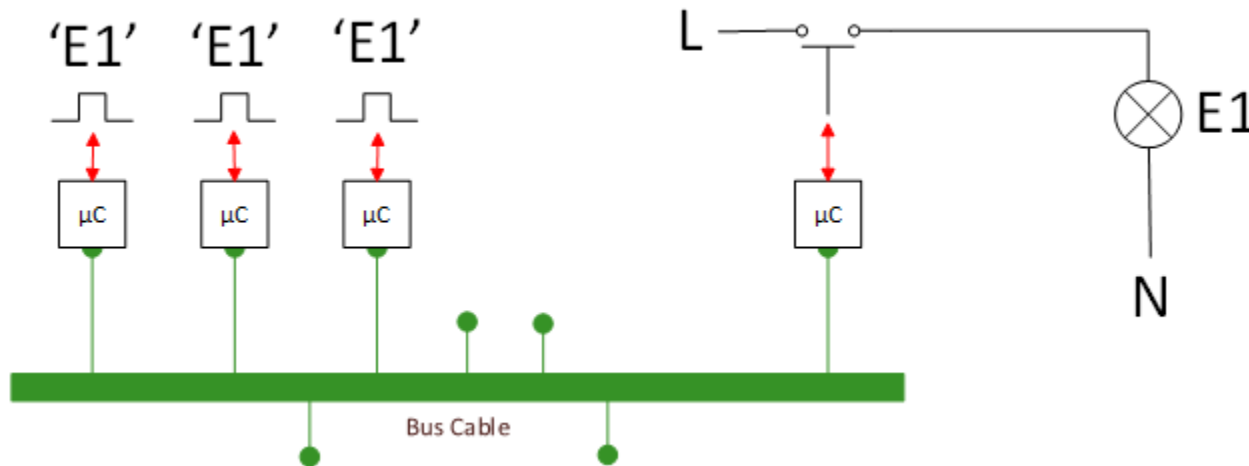

Example

- At one of the push buttons: user manipulation for the 'E1'-rocker
- This sensor broadcasts a message for each such user manipulation
- Each such message has two parameters:
 - Address = 'E1'
 - Value = either 0 or 1
- All sensors & actuators interpret any received message
- All actuators addressed by 'E1' switch E1 accordingly (here only one)


Connections: physical vs. virtual

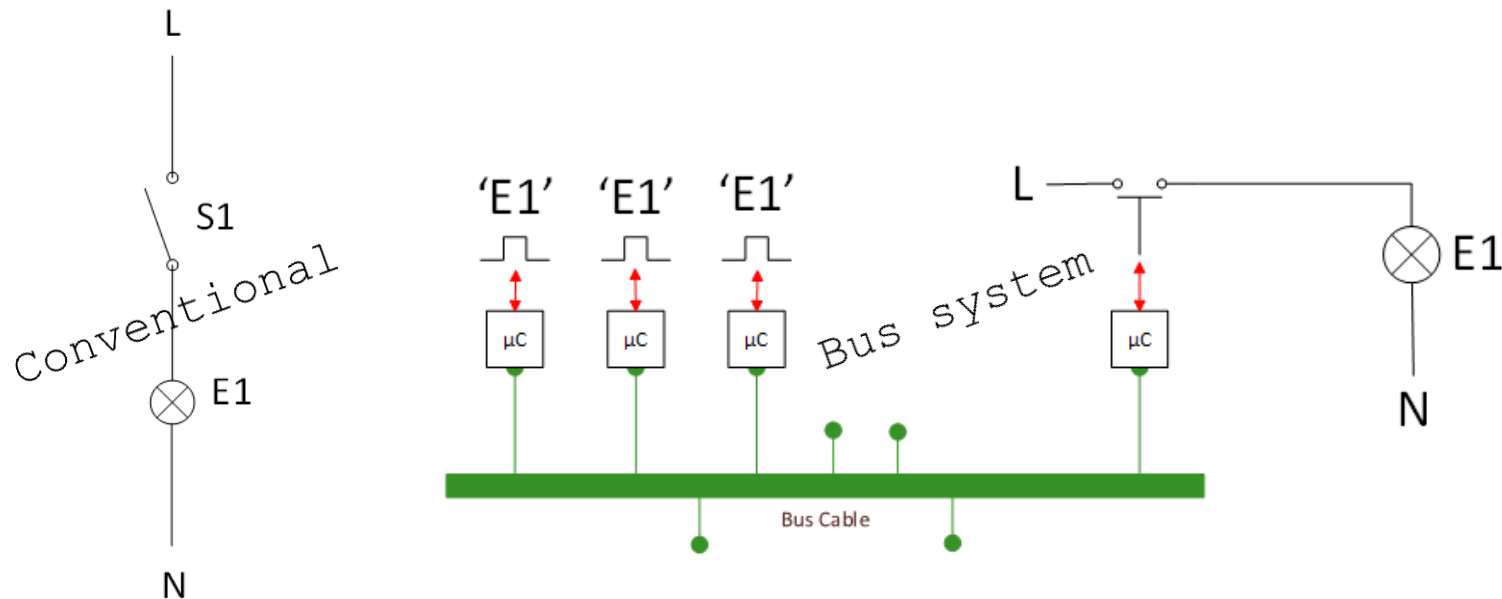

Connection between operating elements & electrical consumers

- **Conventional system:** directly & physically linked via **wires**
- **Bus system:** indirectly, virtually linked via **address** parameters in messages exchanged between μCs

Bus System: practical advantages

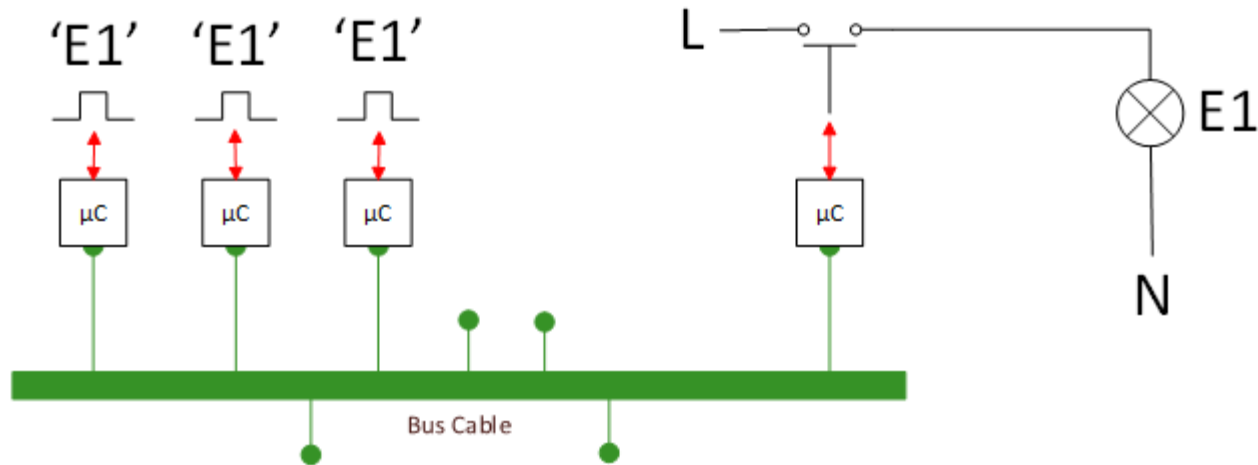


- Cabling = easy = time saving = cheaper
- Optimal functionality/cable ratio
- Flexible: add more sensors and actuators
- Separation between power (230V) & operation

Add more lamps...

The same bus can of course be used for additional lamps

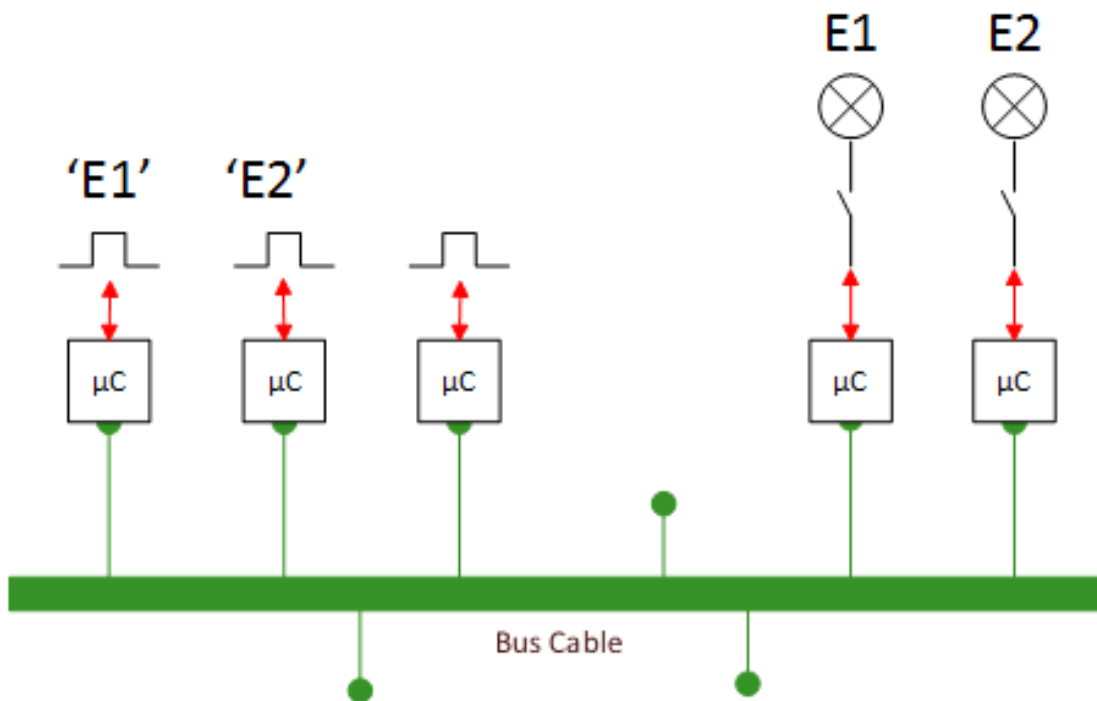
- sensor μC \leftrightarrow E1 pulses \rightarrow actuator μC \leftrightarrow E1 relay
- sensor μC \leftrightarrow E2 pulses \rightarrow actuator μC \leftrightarrow E2 relay



Actuators: combine lamps

One μC can control several electrical consumers

 - sensor μC \leftrightarrow E1 pulses \rightarrow actuator μC \leftrightarrow E1 & E2 relays
- sensor μC \leftrightarrow E2 pulses \rightarrow actuator μC \leftrightarrow E1 & E2 relays




Sensors: combine function types

Sensor μC \leftrightarrow E1 & E4 pulses


→ actuator μC \leftrightarrow E1 & E2 relays: control **light** E1

 → actuator μC \leftrightarrow E3 & E4 relays: control **blind** E4




Bus System: easy modifications...

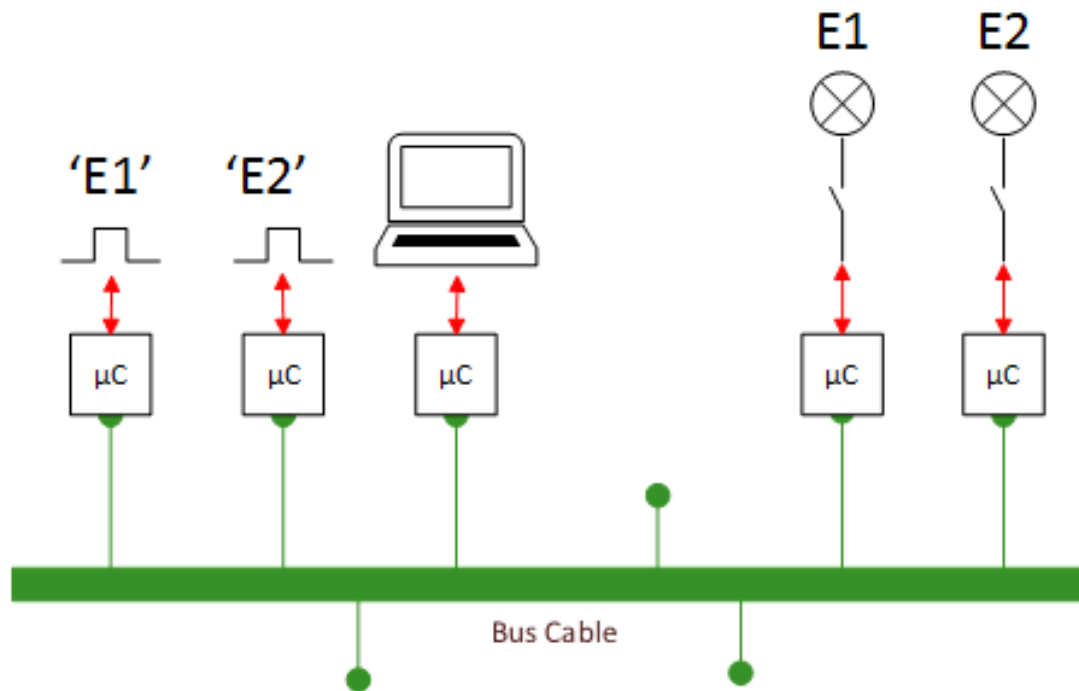- Sensor & actuators exchange runtime messages
- Interfaces exchange management & diagnostic messages
- Interface = μ C connecting the bus to a PC




(re-)programming vs. rewiring

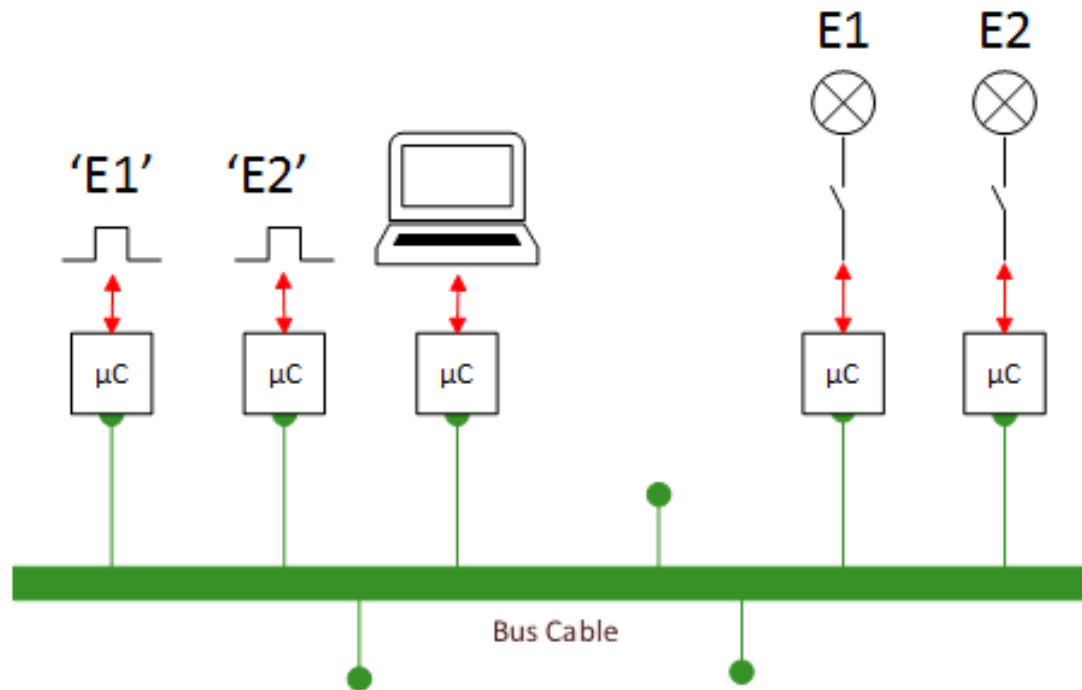- μC functionality = μC memory image
- Changing the μC functionality = changing the μC memory image
- Software tool + PC + interface \rightarrow change μC memory images




With a software tool it's easy to...

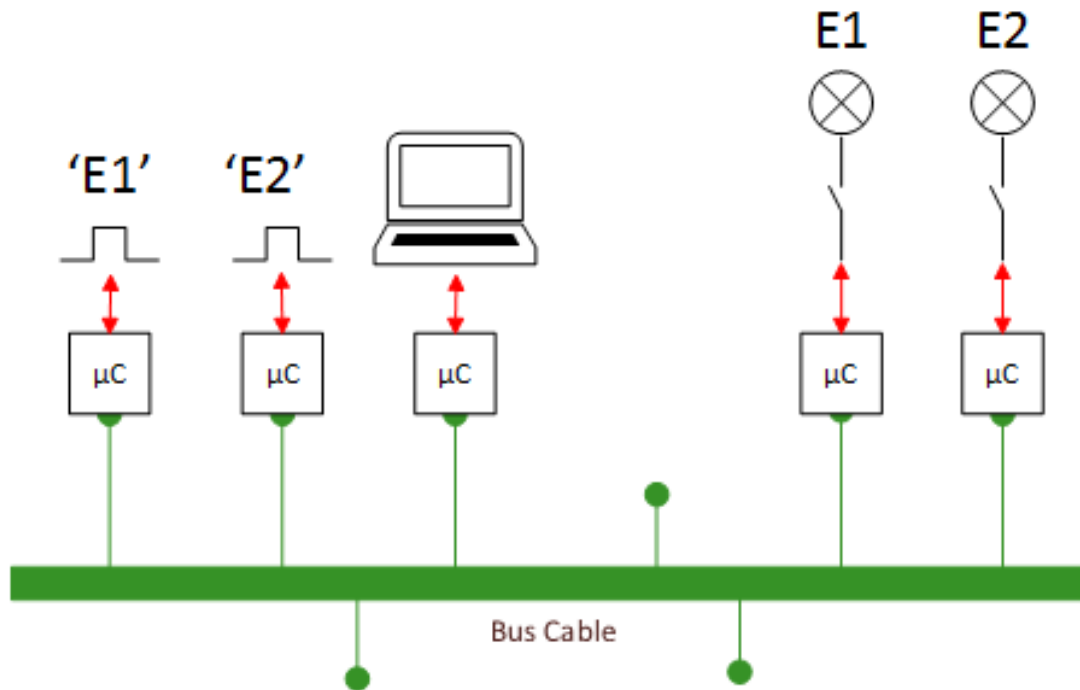- **Fine tune:** e.g. stairway function for E2: automatic (delayed) switch off
- **Modify:** e.g. sensor shall serve E2 instead of E1
- **Add:** e.g. sensor already serving E1 shall also serve E2
- **Extend:** e.g. add a sensor to the installation



KNX + software tool = ETS (*)

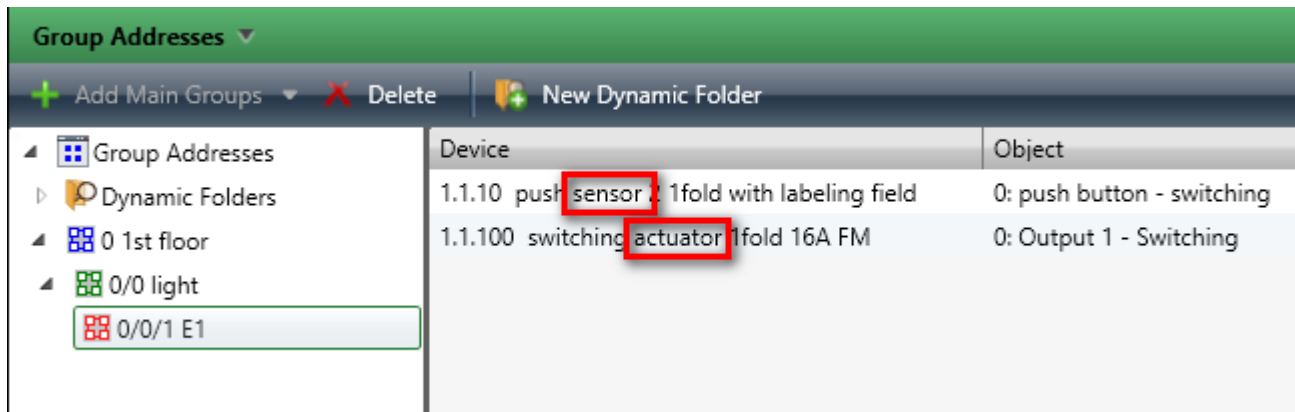- Remember: bus system = sensors & actuators virtually linked
- KNX + virtual link = group address
- E1: group address = 0/0/1
- Sensor: device 1.1.10
- Actuator: device 1.1.100




Device	Object
1.1.10 push sensor 1fold with labeling field	0: push button - switching
1.1.100 switching actuator 1fold 16A FM	0: Output 1 - Switching

(*) More details in 'KNX Basics' webinar: don't hesitate to subscribe!

ETS: add more sensors to E1

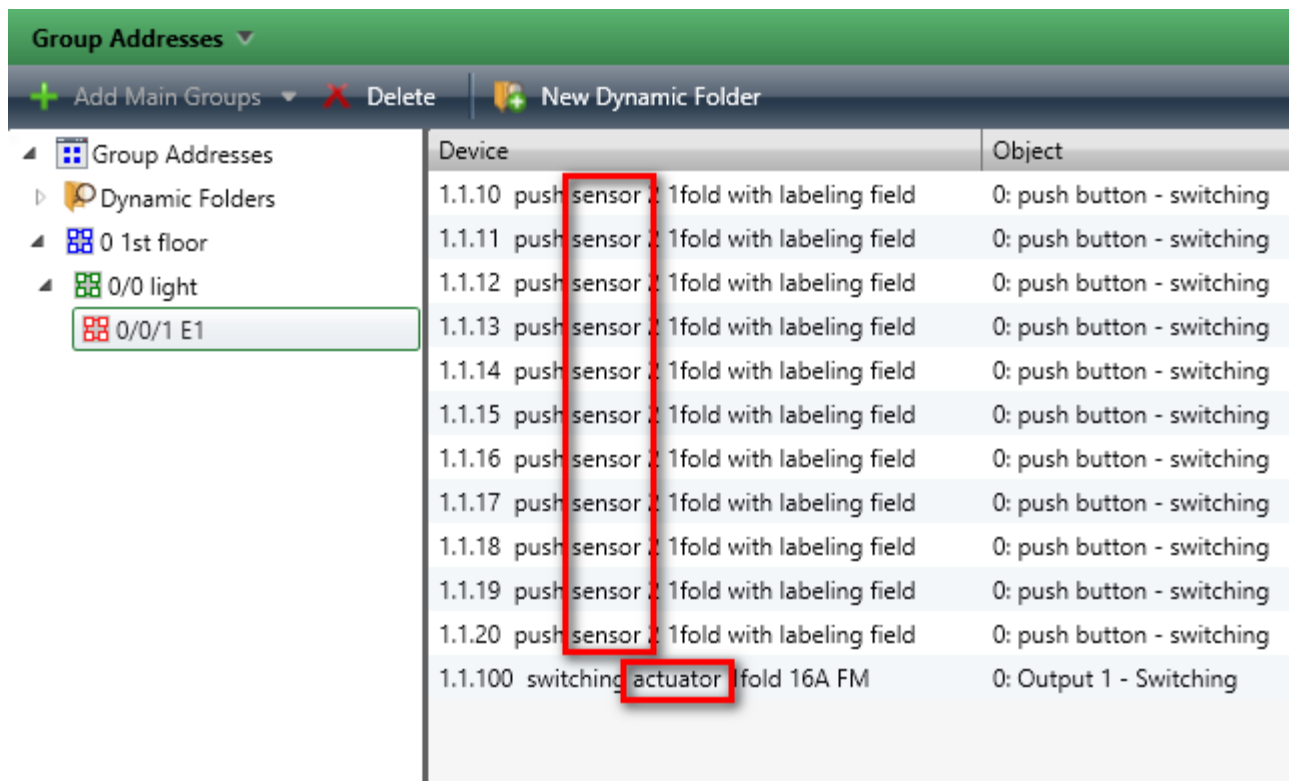
- E1: group address = 0/0/1
- Sensors: devices [1.1.10]..[1.1.20]



Device	Object
1.1.10 push sensor 2 1fold with labeling field	0: push button - switching
1.1.11 push sensor 2 1fold with labeling field	0: push button - switching
1.1.12 push sensor 2 1fold with labeling field	0: push button - switching
1.1.13 push sensor 2 1fold with labeling field	0: push button - switching
1.1.14 push sensor 2 1fold with labeling field	0: push button - switching
1.1.15 push sensor 2 1fold with labeling field	0: push button - switching
1.1.16 push sensor 2 1fold with labeling field	0: push button - switching
1.1.17 push sensor 2 1fold with labeling field	0: push button - switching
1.1.18 push sensor 2 1fold with labeling field	0: push button - switching
1.1.19 push sensor 2 1fold with labeling field	0: push button - switching
1.1.20 push sensor 2 1fold with labeling field	0: push button - switching
1.1.100 switching actuator 1fold 16A FM	0: Output 1 - Switching

ETS: add more actuators to E1

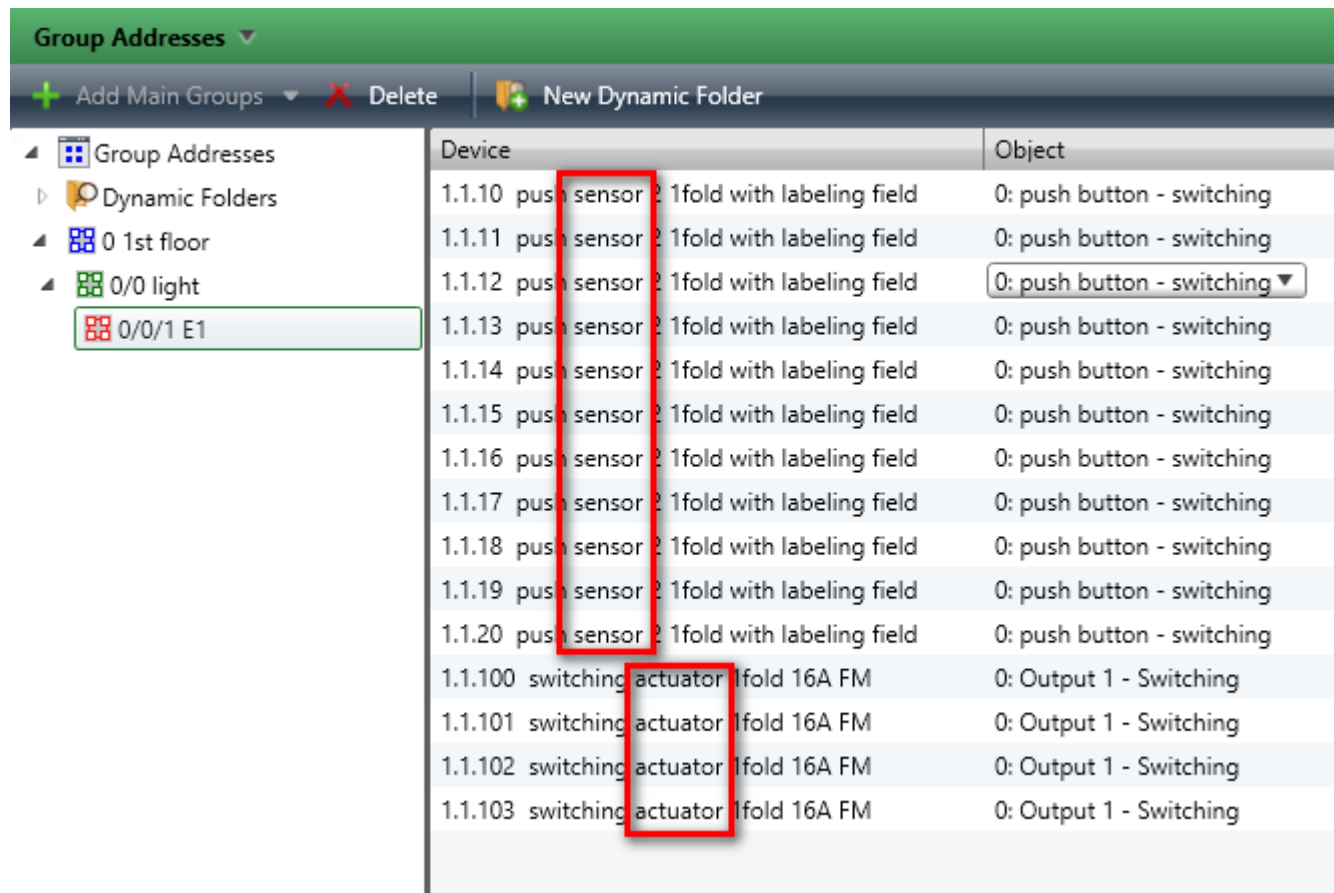- E1: group address = 0/0/1
- Actuators: devices [1.1.100]..[1.1.103]



Device	Object
1.1.10 push sensor 2 1fold with labeling field	0: push button - switching
1.1.11 push sensor 2 1fold with labeling field	0: push button - switching
1.1.12 push sensor 2 1fold with labeling field	0: push button - switching
1.1.13 push sensor 2 1fold with labeling field	0: push button - switching
1.1.14 push sensor 2 1fold with labeling field	0: push button - switching
1.1.15 push sensor 2 1fold with labeling field	0: push button - switching
1.1.16 push sensor 2 1fold with labeling field	0: push button - switching
1.1.17 push sensor 2 1fold with labeling field	0: push button - switching
1.1.18 push sensor 2 1fold with labeling field	0: push button - switching
1.1.19 push sensor 2 1fold with labeling field	0: push button - switching
1.1.20 push sensor 2 1fold with labeling field	0: push button - switching
1.1.100 switching actuator 1fold 16A FM	0: Output 1 - Switching
1.1.101 switching actuator 1fold 16A FM	0: Output 1 - Switching
1.1.102 switching actuator 1fold 16A FM	0: Output 1 - Switching
1.1.103 switching actuator 1fold 16A FM	0: Output 1 - Switching

KNX: the future proof bus system

KNX = quality

- ISO 9001 = prerequisite for product certification

KNX = compatibility

- Compatibility = manufacturer independent
- Assured via product certification

KNX = backwards compatibility

- Extend 20 year old installations with new KNX devices
- Extend today's installations with any future KNX device

KNX = saving energy

- Today: window contacts, presence detection, etc.
- Tomorrow: link KNX installations to smart grids (KNX city)

KNX = the reference bus system

KNX = combining all possible building application types

- Lighting, Shutters/Blinds
- HVAC
- Security
- Metering, Energy management
- Audio/Video, White goods
- etc.

KNX = combining communication media

- TP: the base
- PL: renovation
- IP: high speed and **secure** backbone
- RF: flexibility and self-sustaining sensors (no batteries)

KNX = the reference bus system

KNX = linking to 3rd party systems

- Visualization
- Gateways

KNX = one software tool only

- Software tool: ETS
- ETS compatibility is assured via product certification