

# RESISTIVE CIRCUITS

- SERIES/PARALLEL RESISTOR COMBINATIONS - A TECHNIQUE TO REDUCE THE COMPLEXITY OF SOME CIRCUITS
- LEARN TO ANALYZE THE SIMPLEST CIRCUITS
  - THE VOLTAGE DIVIDER
  - THE CURRENT DIVIDER
- WYE - DELTA TRANSFORMATION - A TECHNIQUE TO REDUCE COMMON RESISTOR CONNECTIONS THAT ARE NEITHER SERIES NOR PARALLEL

# SERIES PARALLEL RESISTOR COMBINATIONS

UP TO NOW WE HAVE STUDIED CIRCUITS THAT CAN BE ANALYZED WITH ONE APPLICATION OF KVL(SINGLE LOOP) OR KCL(SINGLE NODE-PAIR)

WE HAVE ALSO SEEN THAT IN SOME SITUATIONS IT IS ADVANTAGEOUS TO COMBINE RESISTORS TO SIMPLIFY THE ANALYSIS OF A CIRCUIT

NOW WE EXAMINE SOME MORE COMPLEX CIRCUITS WHERE WE CAN SIMPLIFY THE ANALYSIS USING THE TECHNIQUE OF COMBINING RESISTORS...

... PLUS THE USE OF OHM'S LAW

## SERIES COMBINATIONS


$$R_S = R_1 + R_2 + \dots + R_N$$

## PARALLEL COMBINATION



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

$$G_p = G_1 + G_2 + \dots + G_N$$


# FIRST WE PRACTICE COMBINING RESISTORS

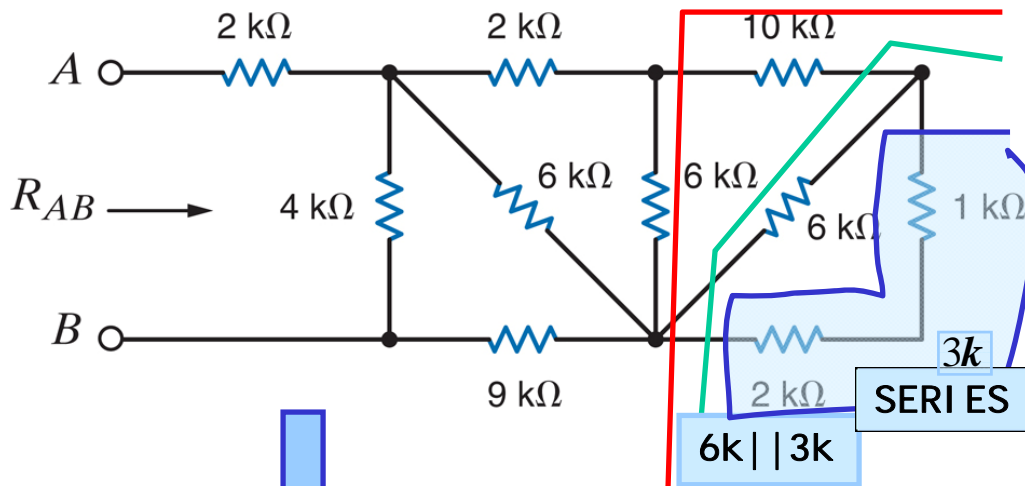


(10K, 2K) SERIES

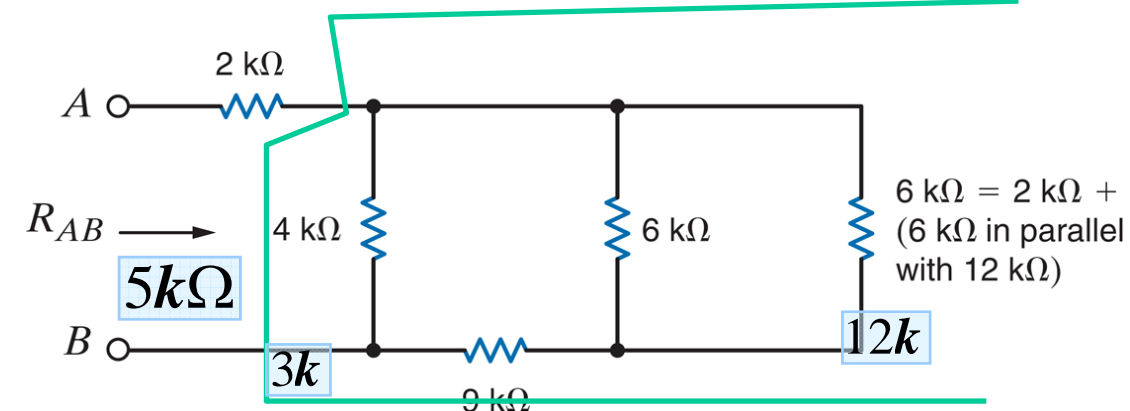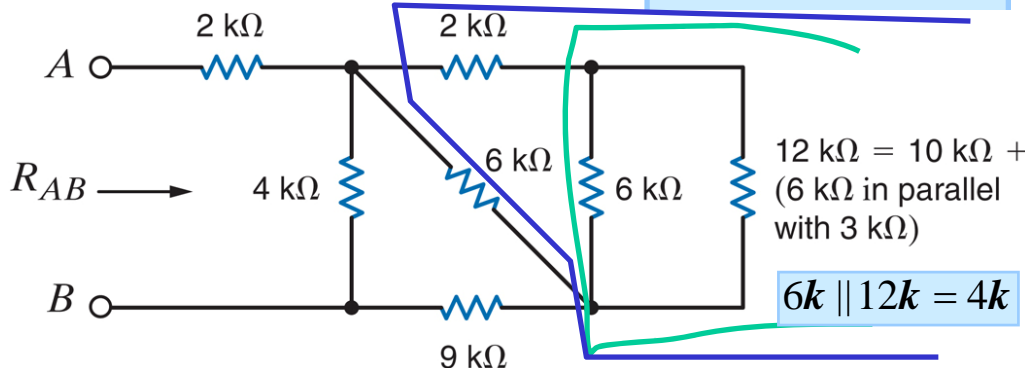

# EXAMPLES COMBINATION SERIES-PARALLEL

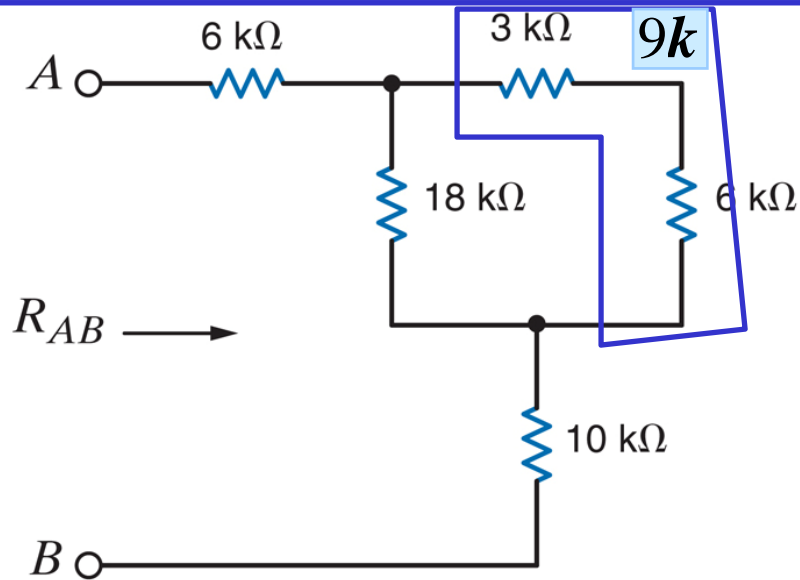

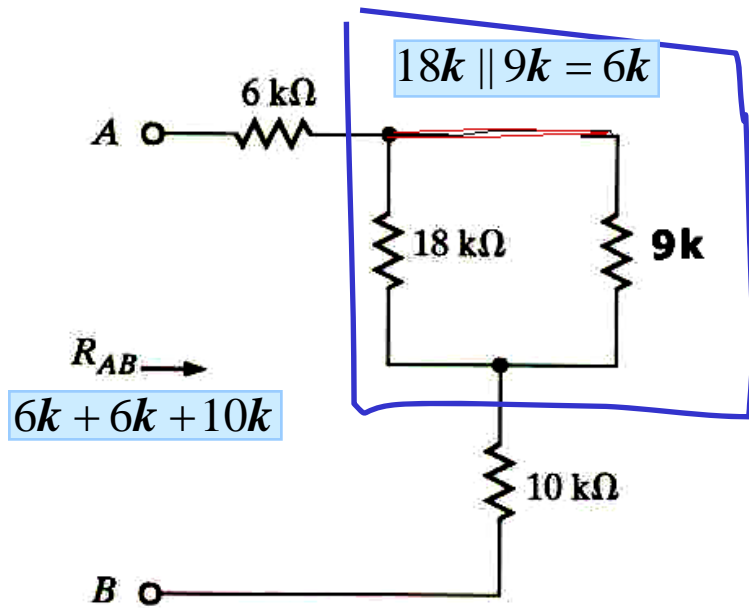
If the drawing gets confusing...  
Redraw the reduced circuit  
and start again



RESISTORS ARE IN SERIES IF THEY CARRY EXACTLY THE SAME CURRENT

RESISTORS ARE IN PARALLEL IF THEY ARE CONNECTED EXACTLY BETWEEN THE SAME TWO NODES

## EFFECT OF RESISTOR TOLERANCE

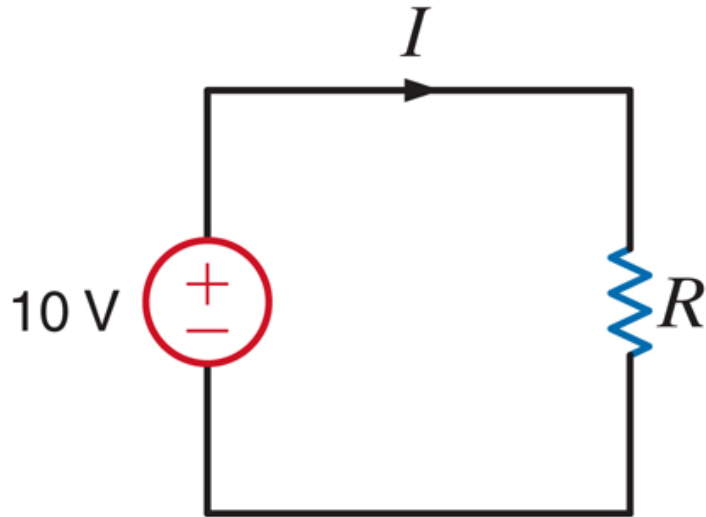

NOMINAL RESISTOR VALUE:  $2.7\text{k}\Omega$   
RESISTOR TOLERANCE: 10%

RANGES FOR CURRENT AND POWER?

$$\text{NOMINAL CURRENT: } \bar{I} = \frac{10}{2.7} = 3.704\text{mA}$$

$$\text{NOMINAL POWER: } P = \frac{(10)^2}{2.7} = 37.04\text{mW}$$

$$\text{MINIMUM CURRENT: } I_{\min} = \frac{10}{1.1 \times 2.7} = 3.367\text{mA}$$

$$\text{MAXIMUM CURRENT: } I_{\max} = \frac{10}{0.9 \times 2.7} = 4.115\text{mA}$$

$$\text{MINIMUM POWER (} V_{I_{\min}} \text{): } 33.67\text{mW}$$

$$\text{MAXIMUM POWER: } 41.15\text{mW}$$

## CIRCUIT WITH SERIES-PARALLEL RESISTOR COMBINATIONS


THE COMBINATION OF COMPONENTS CAN REDUCE THE COMPLEXITY OF A CIRCUIT AND RENDER IT SUITABLE FOR ANALYSIS USING THE BASIC TOOLS DEVELOPED SO FAR.

COMBINING RESISTORS IN SERIES ELIMINATES ONE NODE FROM THE CIRCUIT.  
COMBINING RESISTORS IN PARALLEL ELIMINATES ONE LOOP FROM THE CIRCUIT


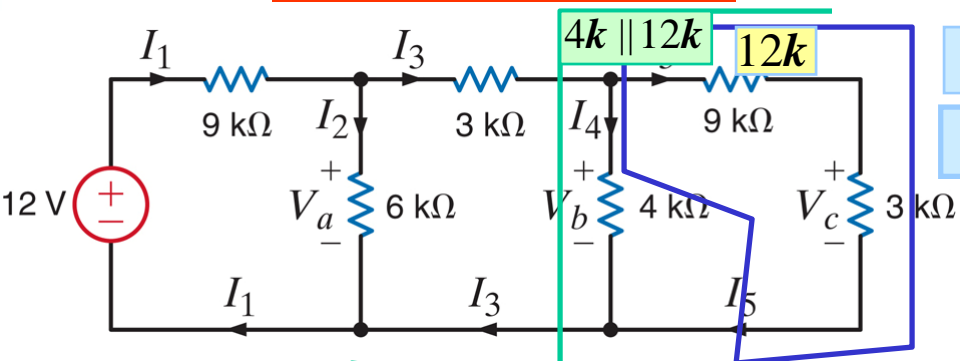
### GENERAL STRATEGY:

- REDUCE COMPLEXITY UNTIL THE CIRCUIT BECOMES SIMPLE ENOUGH TO ANALYZE.
- USE DATA FROM SIMPLIFIED CIRCUIT TO COMPUTE DESIRED VARIABLES IN ORIGINAL CIRCUIT - HENCE ONE MUST KEEP TRACK OF ANY RELATIONSHIP BETWEEN VARIABLES

We wish to find all the currents and voltages labeled in the ladder network shown



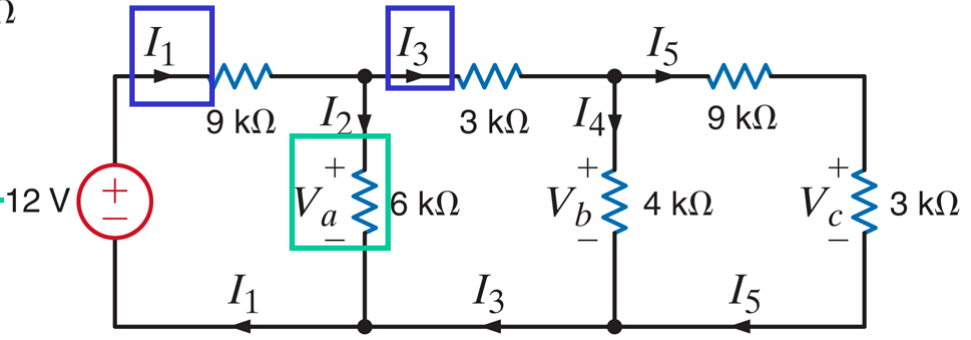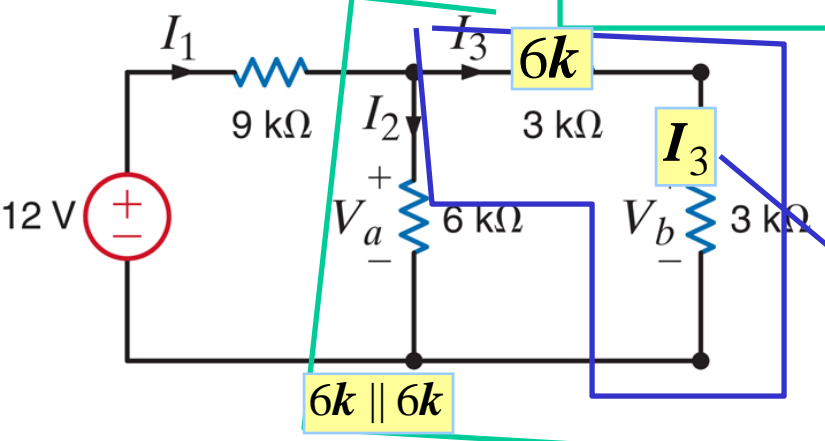FIRST REDUCE IT TO A SINGLE LOOP CIRCUIT  
 SECOND: "BACKTRACK" USING KVL, KCL OHM'S



OHM'S:  $I_2 = \frac{V_a}{6k}$

OHM'S:  $V_b = 3k * I_3$


KCL:  $I_1 - I_2 - I_3 = 0$

...OTHER OPTIONS...

$I_4 = \frac{12}{4+12} I_3$   
 $V_b = 4k * I_4$

KCL:  $I_5 + I_4 - I_3 = 0$

OHM'S:  $V_c = 3k * I_5$

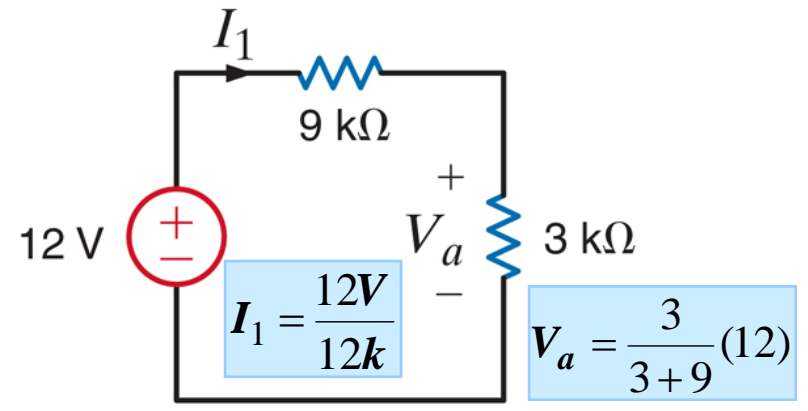


$I_1 = \frac{12V}{12k}$

$V_a = \frac{3}{3+9}(12)$

Find  $V_o$  in the following network:

$$2k \parallel 2k = 1k$$

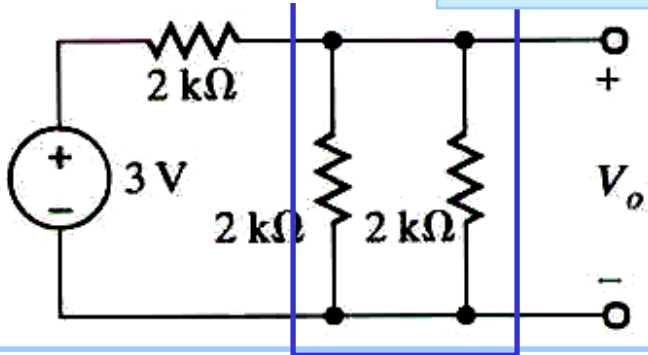


VOLTAGE DIVIDER:  $V_o = \frac{1k}{1k + 2k}(3V) = 1V$

## LEARNING BY DOING

Find  $I_o$  in the following circuit:



$$1k + 1k = 2k$$

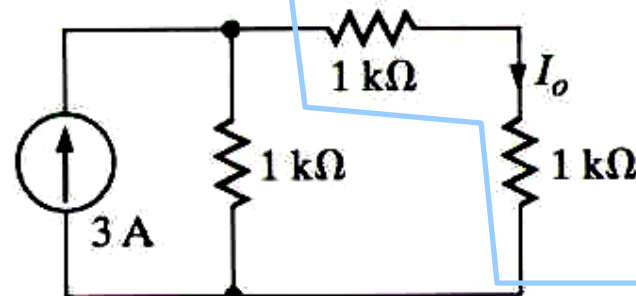

CURRENT DIVIDER:  $I_o = \frac{1k}{1k + 2k}(3A) = 1A$




# Y – Δ TRANSFORMATIONS

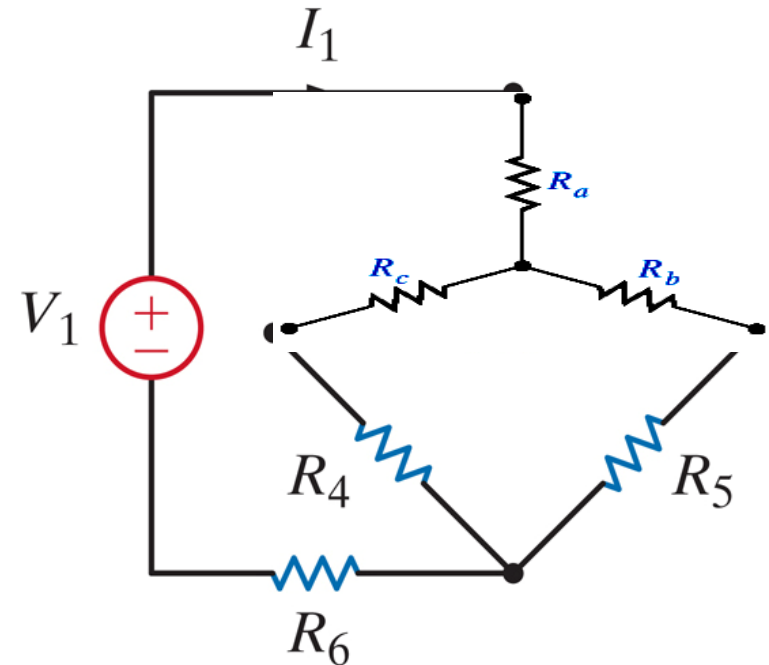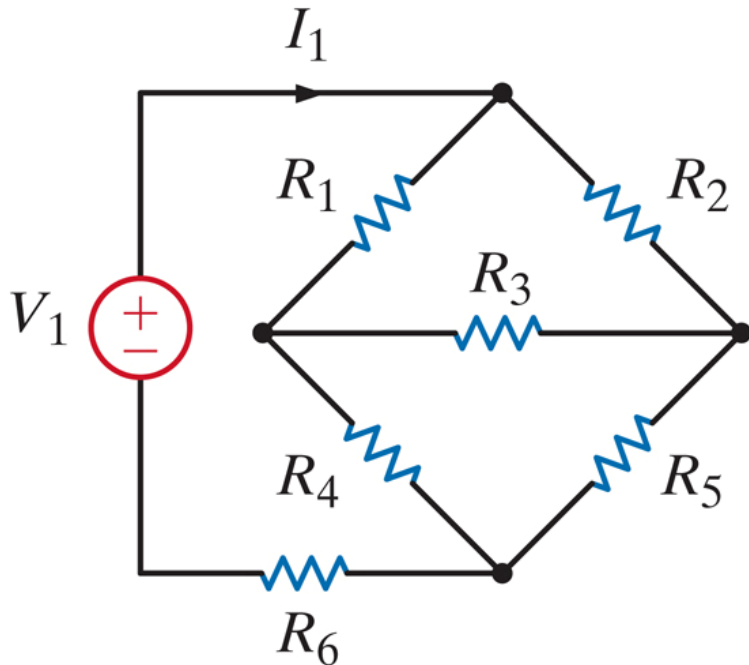


THIS CIRCUIT HAS NO RESISTOR IN SERIES OR PARALLEL


THEN THE CIRCUIT WOULD BECOME LIKE THIS AND BE AMENABLE TO SERIES PARALLEL TRANSFORMATIONS

IF INSTEAD OF THIS

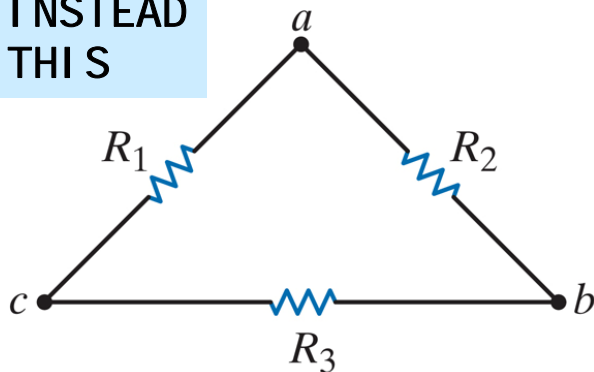

WE COULD HAVE THIS

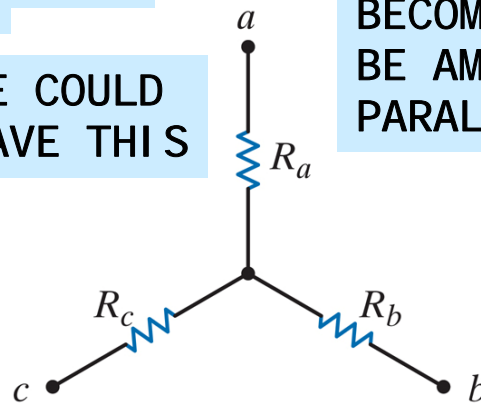

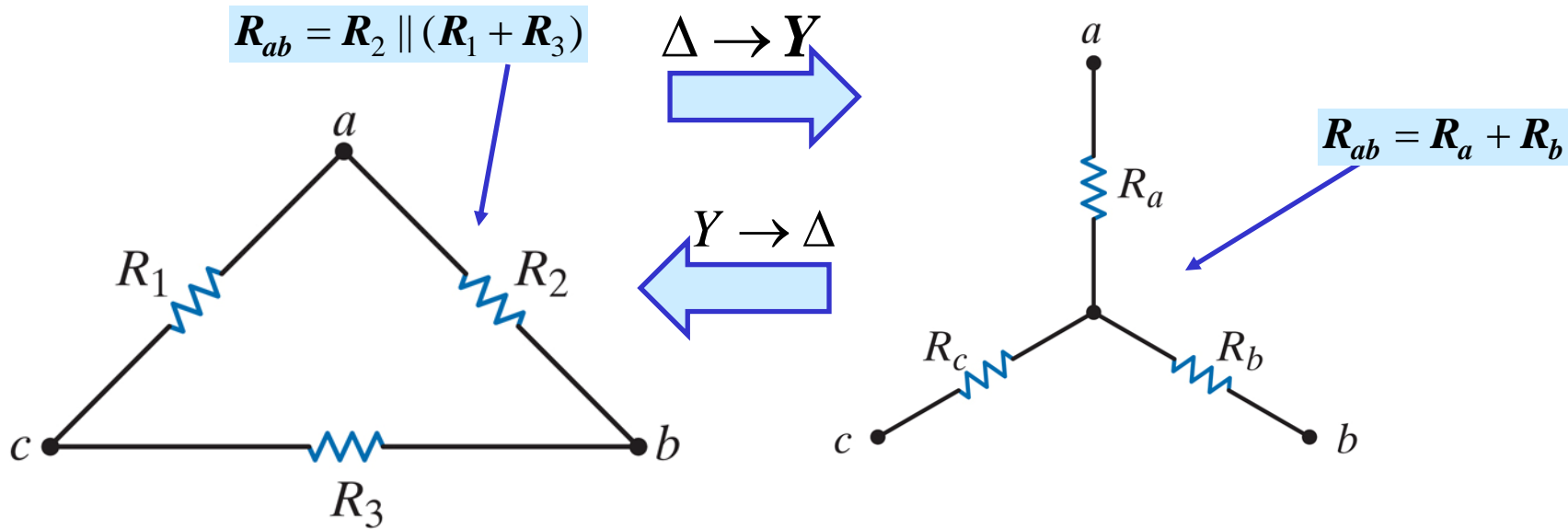

$$R_a + R_b = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$\frac{R_a}{R_b} = \frac{R_1}{R_3} \Rightarrow R_3 = \frac{R_b R_1}{R_a}$$

$$\frac{R_b}{R_c} = \frac{R_2}{R_1} \Rightarrow R_2 = \frac{R_b R_1}{R_c}$$

REPLACE IN THE THIRD AND SOLVE FOR R1

$$R_b + R_c = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_c + R_a = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$


SUBTRACT THE FIRST TWO THEN ADD TO THE THIRD TO GET Ra

$Y - \Delta$

# LEARNING EXAMPLE: APPLICATION OF WYE-DELTA TRANSFORMATION ON

COMPUTE  $I_S$

DELTA CONNECTION

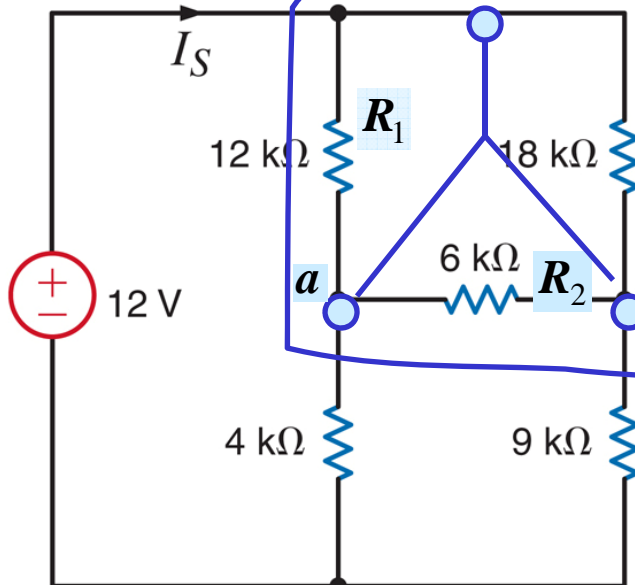


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$\Delta \rightarrow Y$

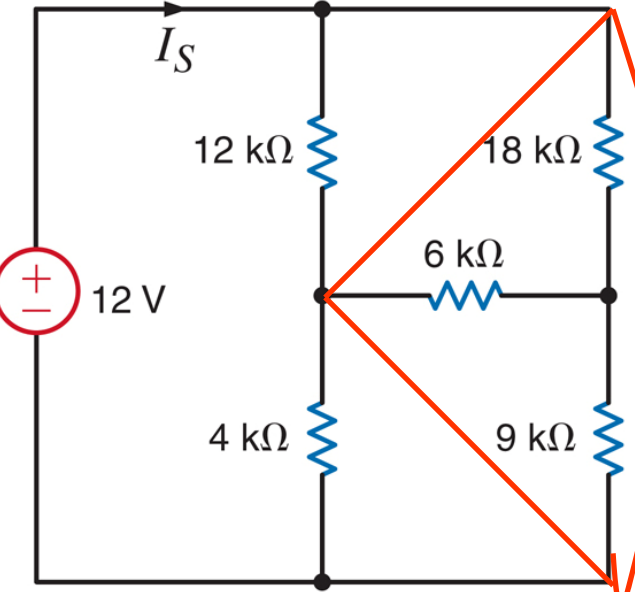

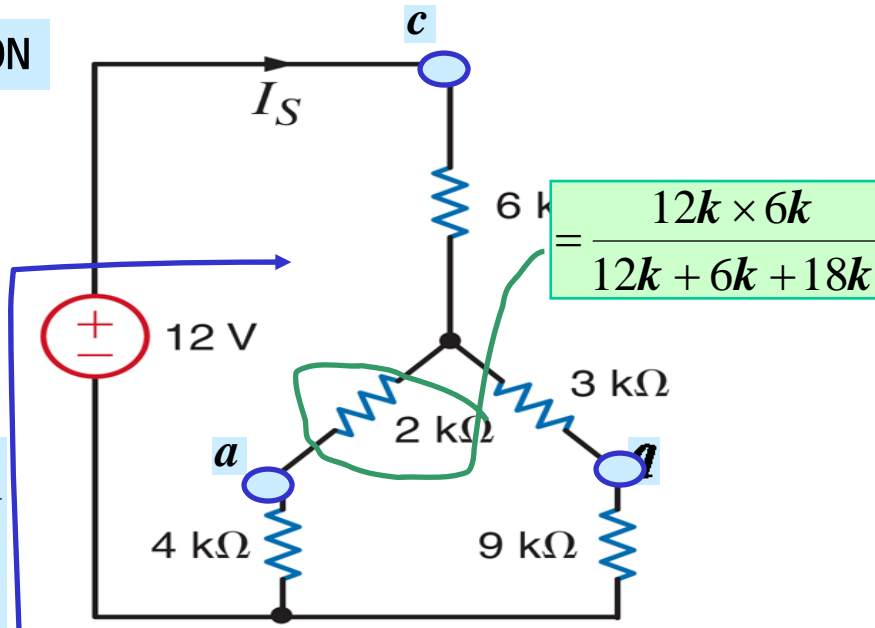ONE COULD ALSO USE A WYE - DELTA TRANSFORMATION ...



$$= \frac{12k \times 6k}{12k + 6k + 18k}$$

$$R_{EQ} = 6k + (3k + 9k) \parallel (2k + 4k) = 10k$$

$$I_S = \frac{12V}{10k} = 1.2mA$$